

Verilog Assignment-1 (CS39001)

Group 6 - 22CS10030, 22CS30046

August 14, 2024

1 Ripple Carry Adder


1.1 Half Adder

1.1.1 Truth Table

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Table 1: Truth Table for Half Adder

1.1.2 Logic Diagram

 

1.1.3 Verilog Code

```
1 module halfadder(s,c,a,b);
2     input a,b;
3     output s,c;
4     xor g1(s,a,b);
5     and g2(c,a,b);
6 endmodule
```

Listing 1: Half Adder Behavioral Style

```

1 module halfadder(s,c,a,b);
2     input a,b;
3     output s,c;
4     xor g1(s,a,b);
5     and g2(c,a,b);
6 endmodule

```

Listing 2: Half Adder Structural Style


1.2 Full Adder

1.2.1 Truth Table

A	B	C_0	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Table 2: Truth Table for Full Adder

1.2.2 Logic Diagram

 

1.2.3 Verilog Code

```

1 module fulladder(s,c,a,b,c0);
2     input a,b,c0;
3     output s,c;
4     assign s = a^b^c0;
5     assign c = a&b | b&c0 | c0&a;
6 endmodule

```

Listing 3: Full Adder Behavioral Style

```

1 module fulladder(s,c,a,b,c0);
2     input a,b,c0;
3     output s,c;
4     wire t1,t2,t3;
5     xor g1(t1,a,b);
6     xor g2(s,c0,t1);
7     and g3(t2,a,b);
8     and g4(t3,t1,c0);
9     or g5(c,t2,t3);
10 endmodule

```

Listing 4: Full Adder Structural Style

1.3 n-bit Adder

 


Figure 1: Ripple Carry Adder

1.3.1 8-bit Adder

Cascade eight Full Adders

```

1 module bitadder8(a, b, cin, s, cout);
2     input [7:0] a, b;
3     input cin;
4     output [7:0] s;
5     output cout;
6
7     wire [8:0] carry;
8     assign carry[0] = cin;
9
10    fulladder FA0 (.a(a[0]), .b(b[0]), .c0(cin), .c(carry[1]), .s(s[0]));
11    fulladder FA1 (.a(a[1]), .b(b[1]), .c0(carry[1]), .c(carry[2]), .s(s[1]));

```

```

12    fulladder FA2 (.a(a[2]), .b(b[2]), .c0(carry[2]), .c(carry[3]),
    .s(s[2]));
13    fulladder FA3 (.a(a[3]), .b(b[3]), .c0(carry[3]), .c(carry[4]),
    .s(s[3]));
14    fulladder FA4 (.a(a[4]), .b(b[4]), .c0(carry[4]), .c(carry[5]),
    .s(s[4]));
15    fulladder FA5 (.a(a[5]), .b(b[5]), .c0(carry[5]), .c(carry[6]),
    .s(s[5]));
16    fulladder FA6 (.a(a[6]), .b(b[6]), .c0(carry[6]), .c(carry[7]),
    .s(s[6]));
17    fulladder FA7 (.a(a[7]), .b(b[7]), .c0(carry[7]), .c(carry[8]),
    .s(s[7]));
18
19    assign cout = carry[8];
20 endmodule

```

Listing 5: 8-bit RCA

1.3.2 16-bit Adder

Cascade two 8-bit Adders

```

1 module bitadder16(a, b, cin, s, cout);
2     input [15:0] a, b;
3     input cin;
4     output [15:0] s;
5     output cout;
6
7     wire [1:0] carry;
8
9     bitadder8 BA8_0 (.a(a[7:0]), .b(b[7:0]), .cin(cin), .cout(carry
    [0]), .s(s[7:0]));
10    bitadder8 BA8_1 (.a(a[15:8]), .b(b[15:8]), .cin(carry[0]), .
    cout(carry[1]), .s(s[15:8]));
11
12    assign cout = carry[1];
13 endmodule

```

Listing 6: 16-bit RCA

1.3.3 32-bit Adder

Cascade two 16-bit Adders

```

1 module bitadder32(a, b, cin, s, cout);
2     input [31:0] a, b;
3     input cin;
4     output [31:0] s;
5     output cout;
6
7     wire [1:0] carry;
8
9     bitadder16 BA16_0 (.a(a[15:0]), .b(b[15:0]), .cin(cin), .cout(
    carry[0]), .s(s[15:0]));
10    bitadder16 BA16_1 (.a(a[31:16]), .b(b[31:16]), .cin(carry[0]),
    .cout(carry[1]), .s(s[31:16]));

```

```

11
12     assign cout = carry[1];
13 endmodule

```

Listing 7: 32-bit RCA

1.3.4 64-bit Adder

Cascade two 32-bit Adders

```

1 module bitadder64(a, b, cin, s, cout);
2     input [63:0] a, b;
3     input cin;
4     output [63:0] s;
5     output cout;
6
7     wire [1:0] carry;
8
9     bitadder32 BA32_0 (.a(a[31:0]), .b(b[31:0]), .cin(cin), .cout(
    carry[0]), .s(s[31:0]));
10    bitadder32 BA32_1 (.a(a[63:32]), .b(b[63:32]), .cin(carry[0]),
    .cout(carry[1]), .s(s[63:32]));
11
12    assign cout = carry[1];
13 endmodule

```

Listing 8: 64-bit RCA

1.4 n-bit Subtractor

Using n-bit Adder, two numbers can be subtracted using the relation:

$$A - B = A + (\sim B) + 1$$

2 Carry Look-Ahead Adder

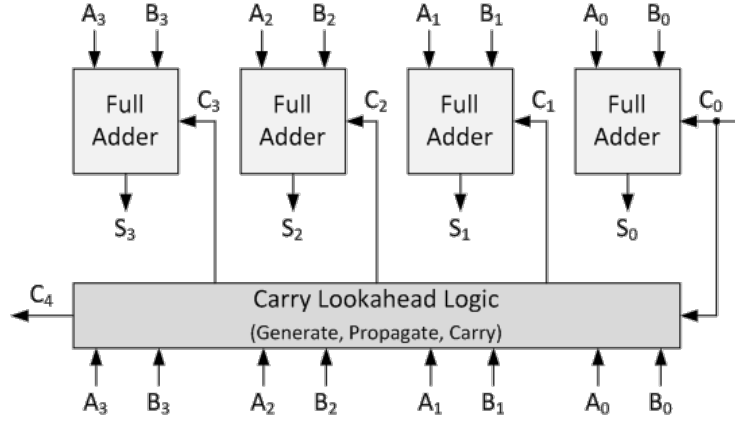


Figure 2: Carry Look-Ahead Adder

2.1 4-bit CLA

2.1.1 Logic Equations

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

$$C_1 = G_0 + P_0 C_{in}$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_{in}$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{in}$$

$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_{in}$$

2.1.2 Verilog Code

```

1 module cla4bit(a, b, cin, s, cout);
2   input [3:0] a, b;
3   input cin;
4   output [3:0] s;
5   output cout;
6
7   wire [4:0] C;
8   wire [3:0] P, G;

```

```

9
10 assign G = a&b;
11 assign P = a^b;
12 assign C[0]=cin;
13
14 assign C[1] = G[0] | (P[0]&C[0]);
15 assign C[2] = G[1] | (P[1]&G[0]) | (P[1]&P[0]&C[0]);
16 assign C[3] = G[2] | (P[2]&G[1]) | (P[2]&P[1]&G[0]) | (P[2]&P[1]&P[0]&C
    [0]);
17 assign C[4] = G[3] | (P[3]&G[2]) | (P[3]&P[2]&G[1]) | (P[3]&P[2]&P[1]&G
    [0]) | (P[3]&P[2]&P[1]&P[0]&C[0]);
18
19 assign s = C[3:0]^P;
20 assign cout = C[4];
21 endmodule

```

Listing 9: 4-bit CLA

2.2 16-bit CLA

2.2.1 Augmented 4-bit CLA

$$\begin{aligned}
 P &= P_3P_2P_1P_0 \\
 G &= G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0
 \end{aligned}$$

```

1 module cla4bit_aug(a, b, cin, s, p, g);
2   input [3:0] a, b;
3   input cin;
4   output [3:0] s;
5   output p, g;
6
7   wire [4:0] C;
8   wire [3:0] P, G;
9
10  assign G = a&b;
11  assign P = a^b;
12  assign C[0]=cin;
13
14  assign C[1] = G[0] | (P[0]&C[0]);
15  assign C[2] = G[1] | (P[1]&G[0]) | (P[1]&P[0]&C[0]);
16  assign C[3] = G[2] | (P[2]&G[1]) | (P[2]&P[1]&G[0]) | (P[2]&P[1]&P[0]&C
    [0]);
17  assign C[4] = G[3] | (P[3]&G[2]) | (P[3]&P[2]&G[1]) | (P[3]&P[2]&P[1]&G
    [0]) | (P[3]&P[2]&P[1]&P[0]&C[0]);
18
19  assign s = C[3:0]^P;
20  assign p = &P;
21  assign g = G[3] | (P[3]&G[2]) | (P[3]&P[2]&G[1]) | (P[3]&P[2]&P[1]&G
    [0]);
22 endmodule

```

Listing 10: Augmented 4-bit CLA

2.2.2 Lookahead Carry Unit

```
1 module lcu(P,G,cin,C);
2   input [3:0] P, G;
3   input cin;
4
5   output [4:0] C;
6
7   assign C[0] = cin;
8   assign C[1] = G[0] | (P[0] & C[0]);
9   assign C[2] = G[1] | (P[1] & G[0]) | (P[1] & P[0] & C[0]);
10  assign C[3] = G[2] | (P[2] & G[1]) | (P[2] & P[1] & G[0]) | (P[2] & P[1] & P[0] & C[0]);
11  assign C[4] = G[3] | (P[3] & G[2]) | (P[3] & P[2] & G[1]) | (P[3] & P[2] & P[1] & G[0]) | (P[3] & P[2] & P[1] & P[0] & C[0]);
12 endmodule
```

Listing 11: Lookahead Carry Unit

2.2.3 Final Module

```
1 module cla16bit(a,b,cin,s,cout);
2   input [15:0] a, b;
3   input cin;
4   output [15:0] s;
5   output cout;
6
7   wire [3:0] P, G;
8   wire [4:0] C;
9
10  cla4bit_aug AUG0(.a(a[3:0]),.b(b[3:0]),.cin(C[0]),.p(P[0]),.g(G[0]),.s(s[3:0]));
11  cla4bit_aug AUG1(.a(a[7:4]),.b(b[7:4]),.cin(C[1]),.p(P[1]),.g(G[1]),.s(s[7:4]));
12  cla4bit_aug AUG2(.a(a[11:8]),.b(b[11:8]),.cin(C[2]),.p(P[2]),.g(G[2]),.s(s[11:8]));
13  cla4bit_aug AUG3(.a(a[15:12]),.b(b[15:12]),.cin(C[3]),.p(P[3]),.g(G[3]),.s(s[15:12]));
14  lcu LCU0(.P(P),.G(G),.cin(cin),.C(C));
15
16  assign cout = C[4];
17 endmodule
```

Listing 12: 16-bit CLA